

Lumped-Constant Line Stretcher For Testing Power Amplifier Stability

To determine the stability of an RF power amplifier, oscillator, or transmitter under harsh conditions, a variable line and fixed attenuator are used to simulate a given VSWR at all phase angles. This article describes a lumped-constant line stretcher using either variable capacitors or inductors.

By E.A. Franke and A.E. Noorani
General Electric Company
Lynchburg, VA 24502

Transmitters employing electron tubes were typically narrowband tuned devices. With the advent of the transistor, the RF power amplifier is capable of wideband operation and must therefore be evaluated for stability to avoid interference with other signals. The spectral purity must be maintained in spite of variations in temperature, supply voltage, or load impedance. For applications such as marine, automotive, or portable operation, the antenna may present a severe mismatch to the power amplifier due to the proximity of foreign objects, environmental corrosion, or a pinched coaxial cable. A most stringent test of stability occurs when the power amplifier operates into a high-Q load such as a narrowband duplexer or cavity filter. Commercial mobile transmitters are typically rated to maintain stability into a 3:1 VSWR even under fluctuations of $\pm 20\%$ in supply voltage.

The power amplifier may be tested into a worse case mismatch at all phase angles. This is easily simulated by connecting the amplifier output to an attenuator followed by an adjustable air line terminated in either an open or a short, (Figure 1). Stability is monitored on a spectrum analyzer connected to a directional coupler placed between the power amplifier and the attenuator. Movement of the air line through one-half wavelength will traverse a complete circle around the Smith Chart. The radius of the circle will depend on the size of attenuator used. The mismatch presented by the artificial load is best described using return loss. The value of return loss is simply twice the attenuation

of the fixed pad, assuming negligible loss in the adjustable air line. The mismatch in terms of standing wave ratio is given as

$$\text{VSWR} = \coth \left[\frac{\text{attenuator (dB)}}{8.686} \right] \quad (1)$$

The radius of the mismatch circle on the normalized Smith Chart intersects the right half of the abscissa at the value of the VSWR.

Recently Roderick Blocksom¹ reported on a binary stepped transmission line formed by numerous lengths of coaxial cable and relays. Below 200 MHz the length of a half-wave adjustable air line (>75 cm) becomes so cumbersome that a continuously-variable, lumped-constant version is needed. This article suggests a stretcher using either variable capacitors or inductors instead of transmission lines.


Lumped-Constant Line Stretcher

Consider the network shown in Figure 2. The input impedance is simply the parallel combination of two series circuits L₁, C₁ and L₂, C₂.

$$Z_{in} = j \frac{\left(\omega L_1 - \frac{1}{\omega C_1} \right) \left(\omega L_2 - \frac{1}{\omega C_2} \right)}{\omega(L_1 + L_2) - \frac{1}{\omega} \left(\frac{1}{C_1} + \frac{1}{C_2} \right)} \quad (2)$$

where $\omega = 2\pi f$.

Figure 1. The spectral stability of a power amplifier may be examined for a mismatch at all phase angles.

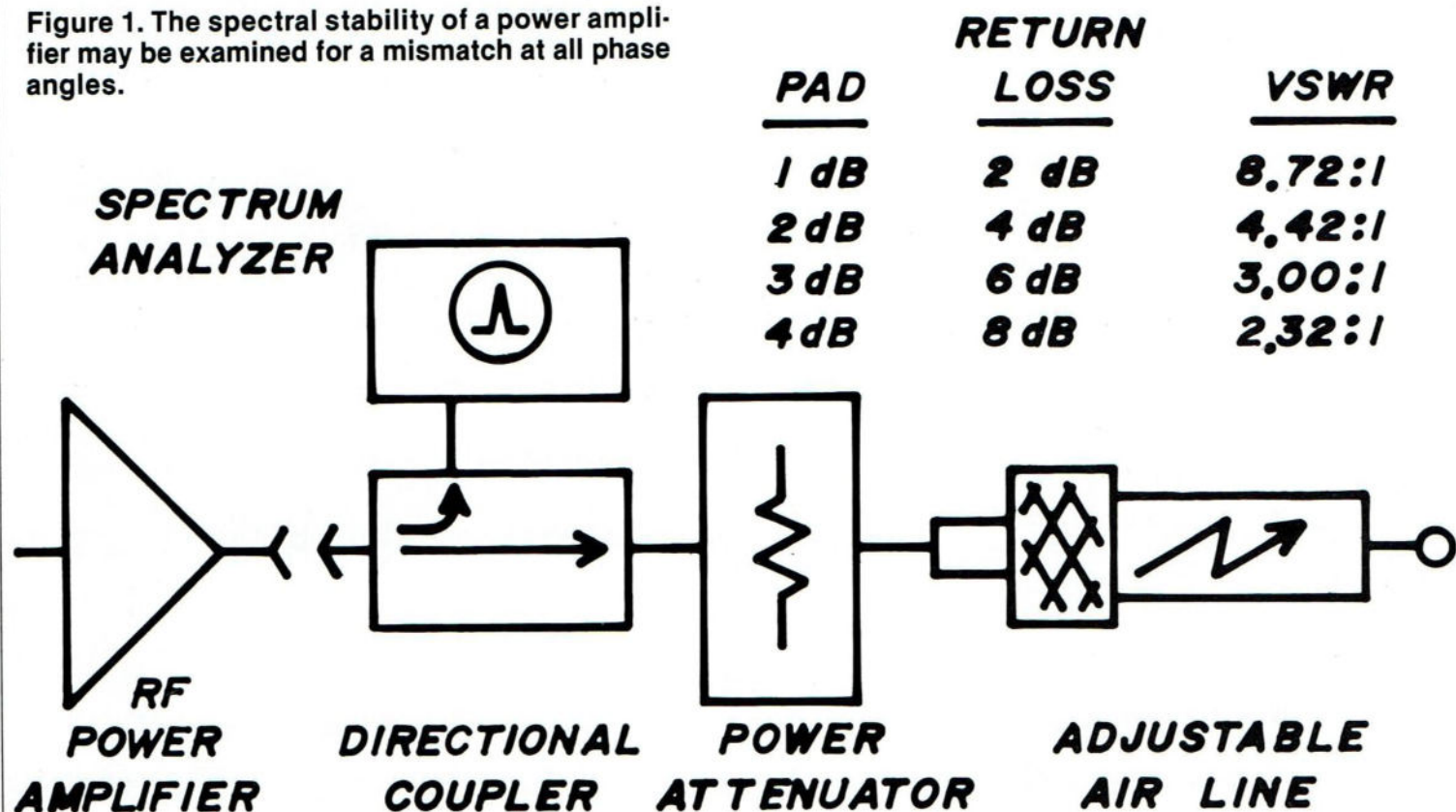

Examination of the above equation shows two zeros in the numerator corresponding to two series resonances. A parallel resonance occurs in the denominator when

$$\omega(L_1 + L_2) = \frac{2}{\omega C} \quad (3)$$

where $C_1 = C_2 = C$ and assuming a ganged dual section or butterfly variable capacitor. The above equation may be rewritten as

$$XC = \frac{XL_1 + XL_2}{2}$$

where $XL_1 = \omega L_1$, $XL_2 = \omega L_2$ and $X_C = \frac{1}{\omega C}$.

At any given frequency, the locus of impedance points plotted on a Smith Chart as the capacitor is varied will be a circle similar to that achieved using a variable length transmission line. If an attenuator is not used, the points will be entirely imaginary ($R = 0$). If an attenuator is used, the value of the real and imaginary parts of the input impedance may simply be read from the chart. When properly designed, as the capacitance is increased, the locus travels from a short circuit (when $XL_1 = X_C$) (Figure 3) to an inductive

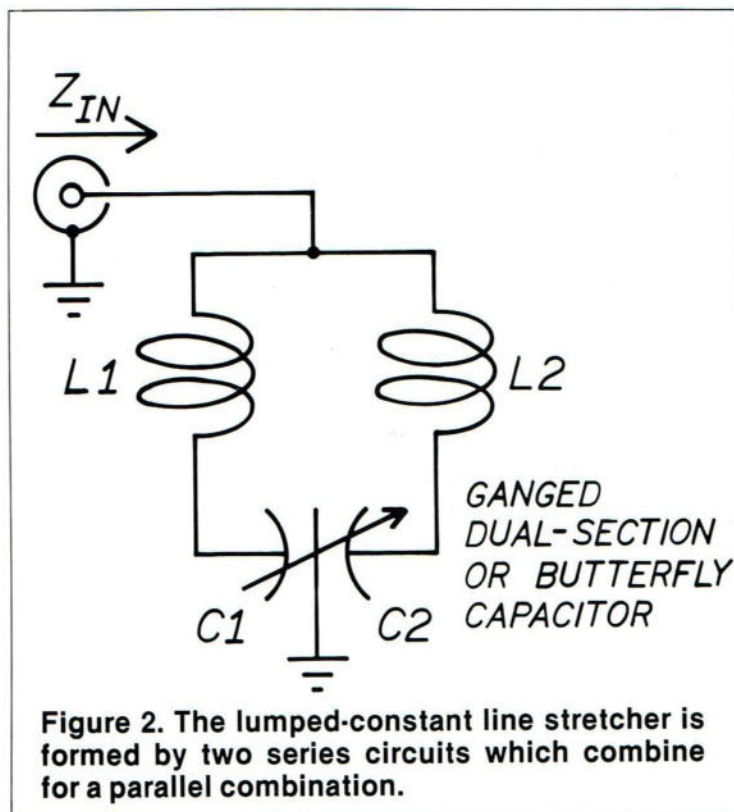


Figure 2. The lumped-constant line stretcher is formed by two series circuits which combine for a parallel combination.

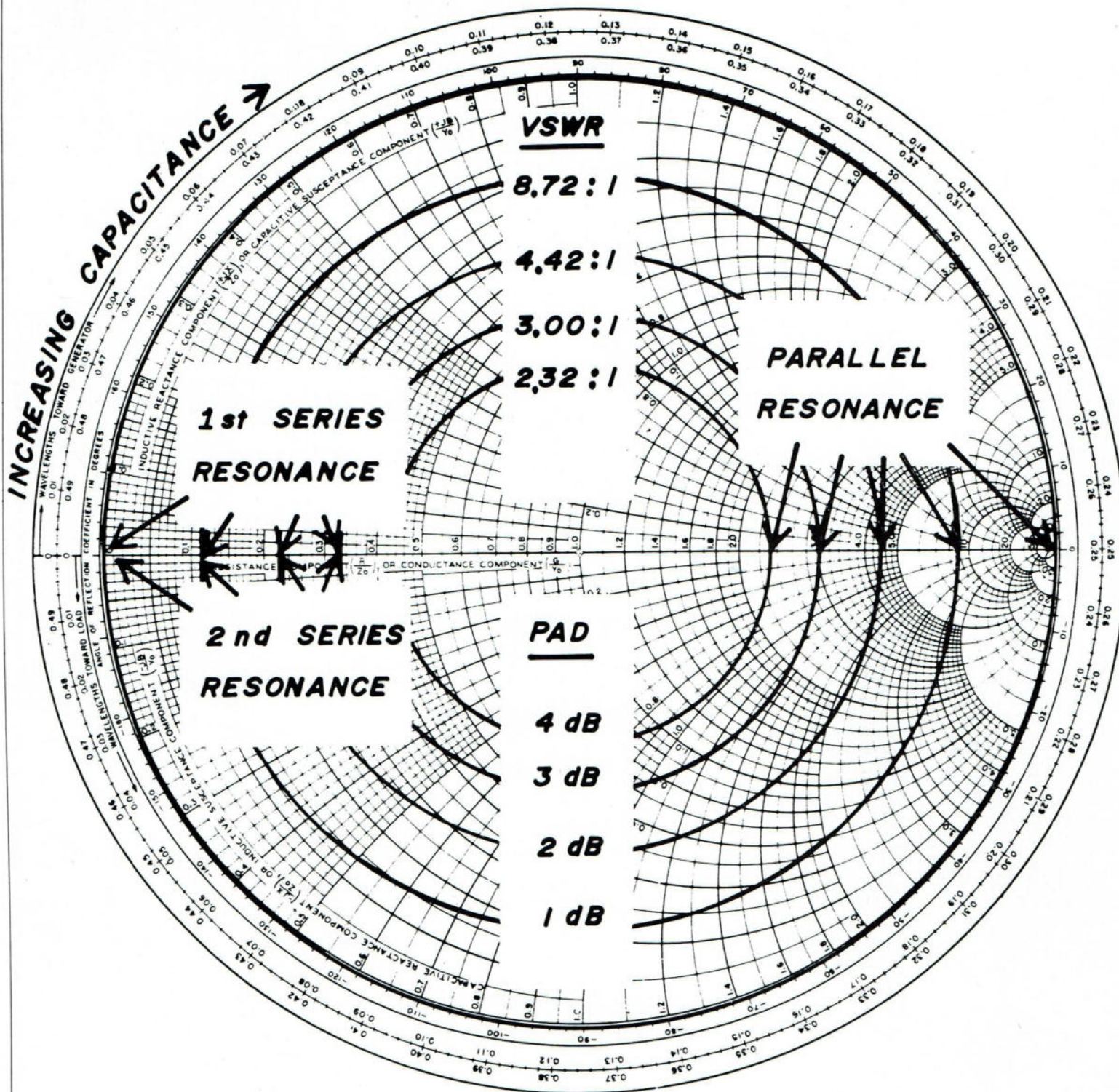


Figure 3. As the variable capacitor is meshed, the loci of input impedance points forms a clock-wise circle of constant VSWR covering all phase angles.

reactance, then through parallel resonance to a capacitive reactance. Finally the locus passes through the second series resonance (when $XL_2 = X_C$) near maximum capacitance.

By properly dictating the end points of the locii at the series resonances, the parallel resonance will occur somewhere between them.

For design purposes, it is necessary to establish the frequency bandwidth over which the lumped-constant variable line has to work. Next the ganged dual-section or butterfly capacitor selected must have a high breakdown voltage and a very high Q. Any dissipative loss in the coil or capacitor will be evidenced by a non-circular response on the Smith Chart. Before any calculations for the inductors are made, the minimum and maximum capacitance should be measured. It is also necessary that the capacitor does not have a self resonance anywhere in the frequency band of interest.

Inductor L_1 is calculated using the maximum capacitance at the lowest operating frequency for series resonance.

$$L_1 = \frac{1}{4\pi^2(F_{\text{low}})^2 C_{\text{max}}} \quad (4)$$

The second inductor L_2 is calculated using the minimum variable capacitance at the highest operating frequency.

$$L_2 = \frac{1}{4\pi^2(F_{\text{high}})^2 C_{\text{min}}} \quad (5)$$

The ratio of inductance L_1/L_2 must be less than unity

$$\frac{L_1}{L_2} = \left(\frac{F_{\text{high}}}{F_{\text{low}}} \right)^2 \left(\frac{C_{\text{min}}}{C_{\text{max}}} \right), \quad (6)$$

which reduces to

$$\left(\frac{F_{\text{high}}}{F_{\text{low}}} \right)^2 < \left(\frac{C_{\text{max}}}{C_{\text{min}}} \right) \quad (7)$$

If the inductors are equal, then parallel resonance will occur at the same time as series resonance both at the highest frequency (C_{min}) and at the lowest frequency (C_{max}).

If the ratio of L_1/L_2 is greater than unity, parallel resonance will not occur within the frequency range F_{low} to F_{high} .

From equation 7, the operating range is limited by the square root of the capacitance ratio. It should be remembered that the input impedance will vary faster when a wider frequency range is chosen. Thus to insure a more gradual change in impedance as the capacitor is rotated, the frequency range is usually limited only to the band of interest.

VHF Example

As an example calculation, a variable line was designed to operate over the two-way radio band, 150 to 175 MHz. A dual variable capacitor was chosen with a minimum capacitance of 7.5 pF and a maximum of 50 pF. We shall limit the range of capacitance to $C_{\text{min}} = 10$ pF and $C_{\text{max}} = 45$ pF to account for parasitic capacitance and to operate slightly away from the capacitor stops.

Get it together...
with BNC and TNC
plugs and receptacles
from **ntt**



Designed to meet military specifications MIL-C39012 for mechanical, electrical and environmental performance, these truly unique coaxial connectors utilize deep drawn brass contacts, precision die cast or machined brass couplings, and unitized one-piece construction (patent pending).

The back crimp design eliminates loose contact pins and reduces connector assembly time by half. Cables are shipped fully assembled, or you may assemble them yourself. Instructions and crimp tools are available.

These coaxial connectors have been tested for a minimum of 500 mating cycles with a maximum mating force of three pounds.

Information about these and threaded and miniature coaxial connectors is available from:

National Tel•Tronics
State Road Hill
Meadville, PA 16335
(814) 724-6440
Telex: NATL TEL MEAD 914-405

ntt
NATIONAL
TEL•TRONICS

$$L_1 = \frac{1}{4 \pi^2 (F_{\text{low}})^2 C_{\text{max}}} = \frac{1}{4 \pi^2 (150 \text{ MHz})^2 (45 \text{ pF})} = 25 \text{ nH}$$

$$L_2 = \frac{1}{4 \pi^2 (F_{\text{high}})^2 C_{\text{min}}} = \frac{1}{4 \pi^2 (175 \text{ MHz})^2 (10 \text{ pF})} = 83 \text{ nH}$$

Very low values of inductance may be simply short lengths of wire or flat copper strips. The exact value is determined by adjusting for series resonance at each end of the capacitor travel.

The input impedance may be quickly examined at band edges. At 150 MHz the first series resonance occurs at $C_{\text{max}} = 45 \text{ pF}$ by the above design. At the second series resonance, the variable capacitor resonates with the other inductor L_2 .

$$XC = XL_2 = 2\pi f L_2 = 2\pi (150 \text{ MHz})(83 \text{ nH}) = 78 \text{ ohms}$$

$$C = \frac{1}{2\pi f X_c} = \frac{1}{2\pi (150 \text{ MHz})(78 \text{ ohm})} = 13.6 \text{ pF}$$

A parallel resonance will occur between the two series resonances when all of the components are taken into account.

$$XC = \frac{XL_1 + XL_2}{2} = \frac{2\pi f (L_1 + L_2)}{2}$$

$$= \pi (150 \text{ MHz})(25 \text{ nH} + 83 \text{ nH}) = 50.9 \text{ ohm}$$

$$C = \frac{1}{2\pi f XC} = \frac{1}{2\pi (150 \text{ MHz})(78 \text{ ohm})} = 20.8 \text{ pF}$$

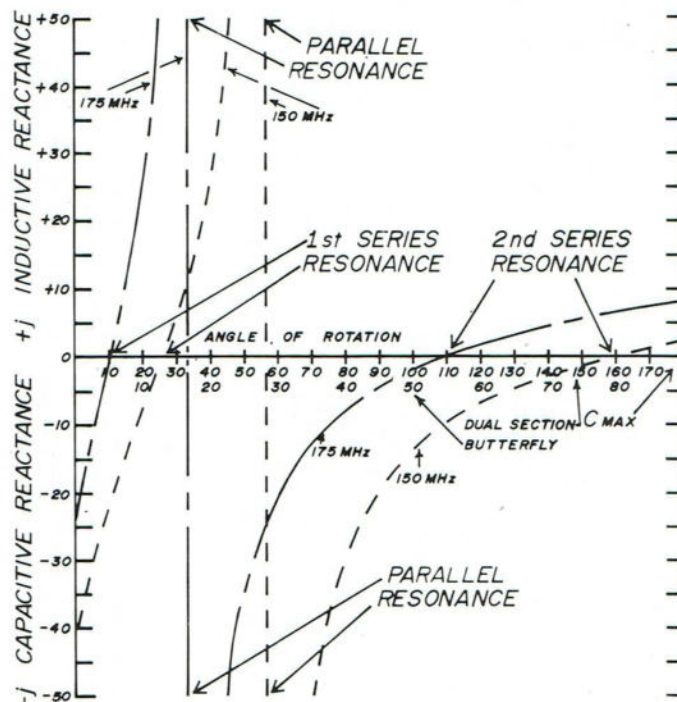



Figure 4.

**LOWEST PRICED, HIGHEST QUALITY ATTENUATORS - BNC \$11.00, SMA \$14.00^{1-9EA}
AND TERMINATIONS - BNC \$5.60^{10EA}, SMA \$5.60^{10EA}, MIL-HI-REL NETWORKS**

Model Number (2)	Impedance Ohms (Power W)	Frequency Range	BNC	TNC	N	SMA	UHF	PC
Fixed Attenuators, 1 to 20 dB								
AT-50(3)	50 (1W)	DC-1.5GHz	14.00	20.00	20.00	18.00	—	12.00
AT-51	50 (1W)	DC-1.5GHz	11.00	15.00	15.00	14.00	—	—
AT-52	50 (1W)	DC-1.5GHz	14.50	20.50	20.50	19.50	—	—
AT-53	50 (25W)	DC-2.0GHz	14.00	17.00	—	15.00	—	—
AT-54	50 (25W)	DC-2.0GHz	—	—	—	18.00	—	—
AT-75 or AT-90	75 or 93 (1W)	DC-1.5GHz	14.00	20.00	20.00	18.00	—	—
Detector, Zero Bias Schottky								
CD-51	50	.01-4.2GHz	—	—	—	54.00	—	—
Resistive Impedance Transformers, Minimum Loss Pads								
RT-50-75	50 to 75	DC-1.5GHz	10.50	19.50	19.50	17.50	—	—
RT-50-93	50 to 93	DC-1.0GHz	13.00	19.50	19.50	17.50	—	—
Terminations:								
CT-50 (3)	50 (1W)	DC-4.2GHz	11.50	15.00	15.00	17.50	—	—
CT-51	50 (1W)	DC-4.2GHz	9.50	12.00	12.00	9.50	—	—
CT-52	50 (1W)	DC-2.5GHz	10.50	15.00	15.00	13.00	15.50	—
CT-53 M	50 (1W)	DC-4.2GHz	5.80 ^{10 Pcs}	—	—	5.80 ^{10 Pcs}	—	—
CT-54	50 (2W)	DC-2.0GHz	14.00	15.00	15.00	17.50	—	—
CT-75	75 (25W)	DC-2.5GHz	10.50	15.00	15.00	13.00	15.50	—
CT-93	93 (25W)	DC-2.5GHz	13.00	15.00	—	—	15.50	—
Mismatched Terminations, 1.05:1 to 3:1, Open Circuit, Short Circuit:								
MT-51	50	DC-3.0GHz	25.50	25.50	25.50	25.50	—	—
MT-75	75	DC-1.0GHz	—	—	25.50	—	—	—
Feed thru Terminations, shunt resistor:								
FT-50	50	DC-1.0GHz	10.50	19.50	19.50	17.50	—	—
FT-75	75	DC-500MHz	10.50	19.50	19.50	17.50	—	—
FT-90	93	DC-150MHz	13.00	19.50	19.50	17.50	—	—
Directional Coupler, 30 dB								
DC-500	50	250-500MHz	60.00	—	—	—	—	—
Resistive Decoupler, series resistor or Capacitive Coupler, series capacitor:								
RD or CC-1000	1000 (1000PF)	DC-1.5GHz	12.00	18.00	18.00	17.00	—	—
Adapters:								
CA-50 (N to SMA)	50	DC-4.2GHz	—	—	13.00	13.00	—	—
Inductive Decouplers, series inductor:								
LD-R15	0.17uH	DC-500MHz	12.00	18.00	18.00	17.00	—	—
LD-6R8	6.8uH	DC-55MHz	12.00	18.00	18.00	17.00	—	—
Fixed Attenuator Sets, 3, 6, 10, and 20 dB, in plastic case:								
AT-50-SET (3)	50	DC-1.5GHz	80.00	84.00	84.00	76.00	—	—
AT-51-SET	50	DC-1.5GHz	48.00	64.00	64.00	60.00	—	—
Reactive Multicouplers, 2 and 4 output ports:								
TC-125-2	50	1.5-125MHz	54.00	—	57.00	57.00	—	—
TC-125-4	50	1.5-125MHz	57.00	—	81.50	81.50	—	—
Resistive Power Dividers, 3, 4 and 9 ports:								
RC-2-30	50	DC-2.0GHz	54.00	—	—	54.00	—	—
RC-3-30	50	DC-500MHz	54.00	—	—	54.00	—	—
RC-9-30	50	DC-500MHz	—	—	—	84.50	—	—
Double Balanced Mixers:								
DBM-1000	50	5-1000MHz	61.00	—	71.00	61.00	—	—
DBM-500PC	50	2-500MHz	—	—	—	—	—	34.00
RF Fuse, 1/8 Amp. and 1.16 Amp.								
FL-50	50	DC-1.5 GHz	12.00	18.00	—	17.00	—	—
FL-75	75	DC-1.5 GHz	12.00	18.00	—	17.00	—	—

NOTE: 1) Critical parameters fully tested and guaranteed. Fabricated from Mil. Spec. High Rel. resistors.
2) See catalog for complete Model Number. Specify connector sizes. Specials available. 3) Calibration marked on label of unit. 4) Price subject to change without notice. Shipping \$5.00 Domestic or \$15.00 Foreign on Prepaid Orders. Delivery is stock to 30 days ARO.

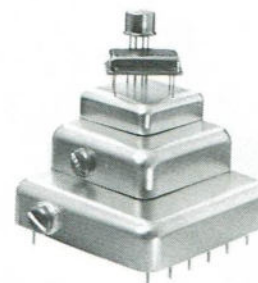Send for Free Catalog on your Letterhead.
Elcom SYSTEMS INC. 305-994-1774
4032 CLINT MOORE ROAD, BOCA RATON, FL 33431



**.001 Hz TO 100MHz
CRYSTAL OSCILLATOR
DIP**

Sizes and Styles Available:

- 4 and 14 pins DIP, CMOS, TTL
A .87" x .50" x .20" C .76" x .46" x .18"
B .80" x .50" x .20"
- TO-5, TO-8, 20 pins flat pack, CMOS, TTL
16 pins DIP. Very low current CMOS.
- Commercial and screened to MIL-STD-883B, MIL-D-55310
- Temperature compensated crystal oscillators (TCXO's)
A. In our standard size 1.50" x 1.50" x .50"
B. Custom designed to your specifications.
- Stabilities Available:
1. $\pm 1 \times 10^{-7}$ (0° to 50°C)
2. $\pm 2 \times 10^{-7}$ (-20° to 70°C)
3. $\pm 5 \times 10^{-7}$ (-40° to 85°C)
4. $\pm 1 \times 10^{-6}$ (-55° to 105°C)

OSCILLATEK

CORPORATION

55755 Foxridge Dr., Mission, Kansas 66202
Tel: (913) 384-2710 Telex: 437045

INFO/CARD 24

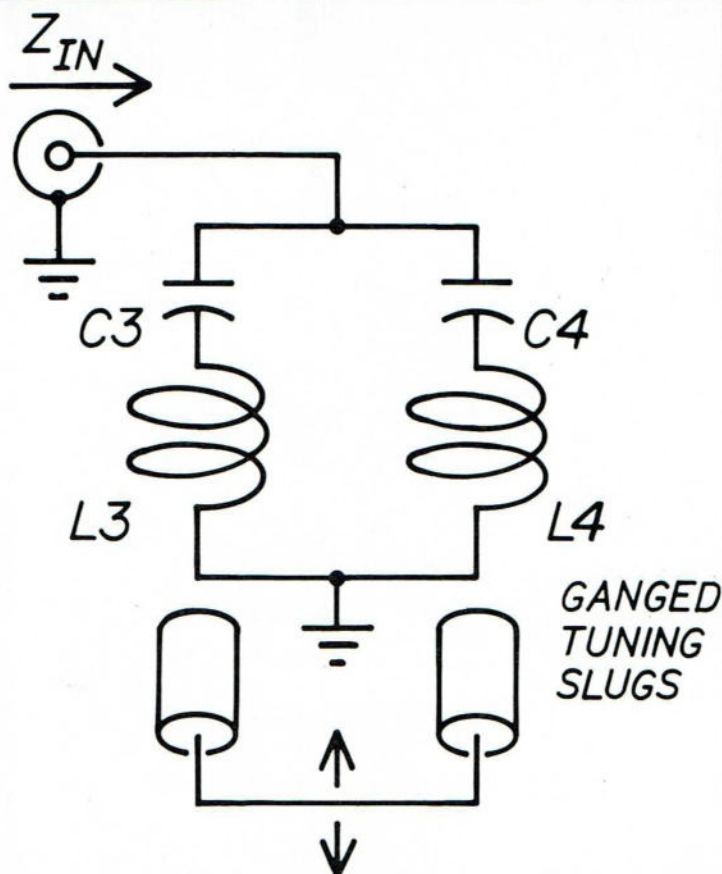


Figure 5. The lumped-constant adjustable line simulator may also be formed using a permeability tuner.

At the high end of the band (175 MHz) the following conditions are present:

First Series Resonance $C = 33 \text{ pF}$

Parallel Resonance $C = 15.3 \text{ pF}$

Second Resonance $C = 10 \text{ pF}$

The input impedance is plotted as a function of capacitor rotation for the lowest and highest operating frequency in Figure 4. Rotation is shown both for a semi-circular (180°) and a butterfly (90°) capacitor. A gear reduction is typically employed with a calibrated dial. The equation for the capacitor is assumed to be linear

$$C = [(\theta/180^\circ)(C_{\max} - C_{\min})] + C_{\min}$$

where

θ = angular rotation in degrees from fully open

$C_{\max} = 50 \text{ pF}$

$C_{\min} = 7.5 \text{ pF}$

The allowable RF power input to this type of device is dependent on the breakdown voltage of the capacitor. For the above design a 500V breakdown capacitor was used and 150 Watts of RF power was applied without any adverse effects.

Variable Inductance Line Stretcher

The variable may be switched from the capacitor to the inductor (Figure 5). A slug formed from ferrite, brass, copper, or aluminum may be mechanically positioned within two identical inductors to vary the inductance. The fixed capacitors, C3 and C4, are computed in a similar manner as above. The conductive metallic core acts as a single shorted turn to decrease the inductance with increased penetration. The powdered iron or ferrite core has the opposite effect

Cost-effective, reliable filter solutions to RFI/EMI problems




LMI manufactures a broad line of high performance, long life power and communications line filters, filter panels, and power factor correction networks. These are now widely used in shielded rooms, data processing centers, communications centers, hospitals, ground support facilities, shielded cabinets and other secure or RF controlled areas. Our power line filters are

designed and manufactured to MIL-F-15733E, UL and other specs; our communications line filters exceed MIL-STD-HBK-232. All models have standard power systems, voltages, current and frequency ratings for easy interface with circuit breakers and UL and NEC requirements.

Write or call for catalog F-300. LECTROMAGNETICS, Inc. 6056 West Jefferson Blvd. Los Angeles, CA 90016 (213) 870-9383

LMI  **LectroMagnetics, Inc.**

INFO/CARD 46

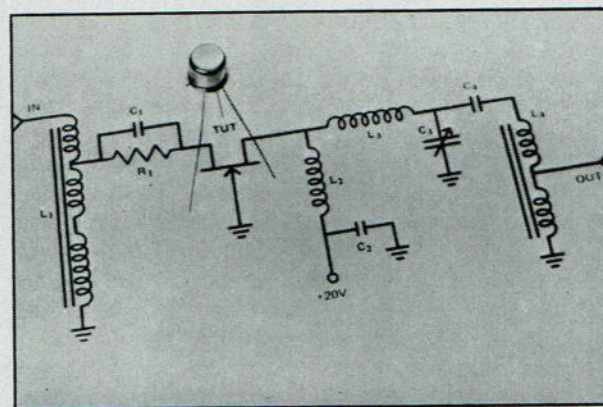

HIGH VOLTAGE BROADBAND RF FET

High dynamic range RF FET now available up to 50V BVDGO, for use with 24 & 32V supplies, and where higher drain voltage improves dynamic range. The CP664 (30V), CP665 (40V), and CP666 (50V) have third order intermodulation intercept $> +40 \text{ dBm}$, and 50 Ohm VSWR < 1.5 to 1 over 0.5 to 50 MHz range.

HIGH VOLTAGE RF FET

 **TELEDYNE CRYSTALONICS**

147 Sherman Street, Cambridge, MA 02140
Tel: (617) 491-1670 • TWX 710-320-1196

INFO/CARD 47

and increases the inductance as it penetrates the coil. The Q of the coil is not appreciably lowered when using the brass slug provided the slug has a clean surface or is silver plated. The use of the powdered iron or ferrite core will raise the Q of the coil provided the material has been selected for the frequency range in use. Ferrite and powdered iron are typically usable up to 200 MHz.

Variable Inductor Example

When a slug having a permeability of μ is inserted into an air-core inductance L_{air} , the final inductance becomes $\mu L_{air} = L_{core}$. Thus L_{core} and L_{air} are the maximum and minimum values of inductance.

If the minimum and maximum of the matched coils are chosen for example to be $L_{max} = L_{core} = 83 \text{ nH}$ and $L_{min} = L_{air} = 25 \text{ nH}$, the values of capacitance may be then calculated.

$$\mu = \frac{L_{core}}{L_{air}} = \frac{83 \text{ nH}}{25 \text{ nH}} = 3.3, \text{ ferrite}$$

$$C_3 = \frac{1}{4\pi^2 (F_{low})^2 L_{max}}$$

$$C_4 = \frac{1}{4\pi^2 (F_{high})^2 L_{min}}$$

For the frequency range of 150 to 174 MHz, $C_3 = 13.56 \text{ pF}$ and $C_4 = 33.08 \text{ pF}$. Parallel resonance will occur when

$$2\omega L = \frac{1}{\omega} \left(\frac{1}{C_3} + \frac{1}{C_4} \right)$$

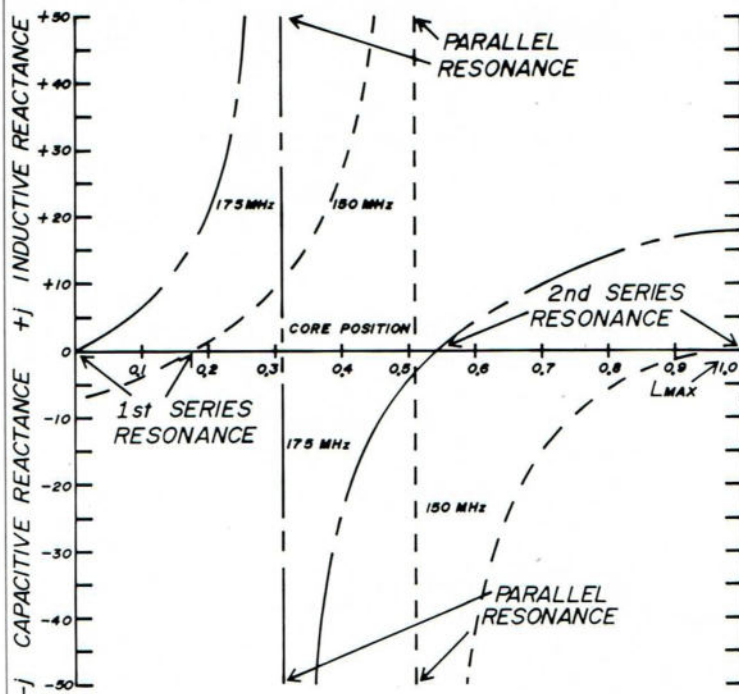


Figure 6. The input for the variable inductor is similar to the previous case as the ferrite slug is inserted into the coil.

"Leader in the Placement
of RF Engineering Professionals"
Call Toll Free 1-800-433-2160

RF Design Engineers (3)

Join the R&D department of this leading CATV products firm. Need 7+ years RF experience in consumer products or CATV equipment. Rocky Mountain location. Salary to mid-50's.

Director of Engineer

Direct the engineering activities of this small, very stable RF communication systems and equipment firm. Knowledge of C-I, ESM, ECM, COMINT SIGINT helpful. Florida location. Salary to mid-50's + equity position.

Senior Microwave Engineer

Rapidly expanding microwave equipment manufacturer needs Engineer to design GaAs FET low noise small signal amps with frequency range up to 10 GHz. Position has high visibility with opportunity to move into management quickly. Southwest location. Salary to mid-40's.

Engineers (many openings)

BSEE, 3+ years in microwave/RD field. Experience designing GaAs FET amps above 1 GHz. Must have knowledge of test instruments in frequencies above 3 GHz. R&D environment. California and East Coast locations. Salary \$30-55k.

RF Engineers (many openings)

If you have a background in communication, navigation, radar or EW systems for military applications, this thriving East Coast firm has a place for you. Positions include Design Engineer, Senior Staff Section Head, Sales Support, Deputy Manager, and Program Manager. Salary to 50's.

RF Design Engineer

Rapidly growing manufacturer of two-way communications equipment needs individual with BSEE and 2+ years experience. North Central U.S. location. Salary to high-30's.

RF Design Engineer

BSEE with 4+ years experience. Will design and develop RF analog circuitry for VHF baseband video system in 5 to 60 MHz range. Salary to \$50k.

Fees Paid—Confidential & Professional

JIM YOUNG & ASSOCIATES

One Young Plaza, Weatherford, TX 76086

Call for information about these and our many other opportunities nationwide.

IN TEXAS CALL COLLECT (817) 599-7623

HIGH DYNAMIC RANGE

RF AMPLIFIERS



Janel offers a wide variety of high dynamic range RF Amplifiers. The chart below shows a sampling of what's available. All feature high *guaranteed* performance and yet are competitively priced. Many models are available from stock.

Model	Frequency	Gain	N.F.	3rd I.P.
PF811	0.1-32 MHz	17.5dB	4.5dB	+42dBm
PF749-1	146-174	16.5	4.0	+35
PF804	215-320	27	4.0	+35
PF7410C	406-512	16.5	4.5	+35
PF797A	800-960	19.5	5.0	+35


In addition to RF Amplifiers, Janel manufactures a wide range of standard Power Dividers and other rf components. Custom designs can be provided for unusual applications. For detailed information, call or write Janel Laboratories, Inc., 33890 Eastgate Circle, Corvallis, OR 97333. Telephone (503) 757-1134.



JANEL LABORATORIES

INFO/CARD 48

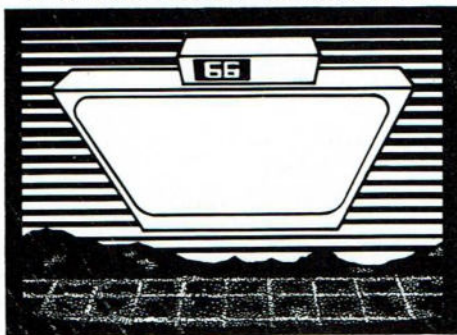"THE WIRED CITY" Jerrold's Technology Will Be There!



Tomorrow's communications systems promise to increase the speed and efficiency of people's day-to-day activities. Working, shopping, information gathering, even voting, will be handled from people's home through high technology electronics.

This concept, called "The Wired City," is fast becoming reality because of the efforts of Jerrold Div. of General Instrument Corp. We're expanding on our recognized leadership in the Cable TV industry and advancing to new frontiers in communications technology. We're presently offering junior through project level openings for the following:

RF DESIGN ENGINEERS

Subscriber Systems

Requires 3 to 5 years' experience in the design/development of RF circuitry. Familiarity with tuners, oscillators, video and RF amplifiers, and phase locked loops a must. Digital design background highly desirable.

RF DESIGN ENGINEERS

CATV Distribution Systems

Requires involvement in design of broadband linear amplifiers, AGC/ALC RF amplifiers, hybrid splitters/couplers, filters and equalizers. Requires 3 to 5

years' solid experience in RF and/or interest in CATV electronic systems development, plus a BSEE or equivalent.

SENIOR CIRCUIT DESIGN ENGINEERS

Advanced R&D Group

Requires "hands-on" R&D applications, focusing on encoding analog signals and encrypting digital signals. Frequency range video and RF to 1 GHz. Requires 3 years' experience building breadboards of analog or digital circuits from discrete components and standard integrated circuits. BSEE or equivalent mandatory.

Our divisional HQ is located in a beautiful, rural suburb of Philadelphia. The area offers fine schools, affordable housing, proximity to an exciting metropolitan area and easy access to resort areas like the Pocono Mountains and New Jersey Seashore.

We offer an excellent salary, a full range of benefits (including paid relocation), and real advancement potential with a dynamic group developing the mass medium of tomorrow. Qualified applicants should write or call (Collect): **Rich Keyser, Dept. RF-1, JERROLD DIVISION, General Instrument Corp., 2200 Byberry Rd., Hatboro, PA 19040, (215) 674-4800.** An Equal Opportunity Employer, M/F/H/V.

Jerrold Division

**GENERAL
INSTRUMENT**

At the low frequency of 150 MHz the value of each inductor will be

$$L = \frac{C_3 + C_4}{2\omega^2 C_3 C_4} = 58.5 \text{ nH}$$

for parallel resonance. The value of each inductor will be 43 nH for parallel resonance at 175 MHz. This is plotted in Figure 6. The abscissa is plotted as linear travel for the position of a ferrite slug into a cylindrical, linearly-wound coil whose dimensions equal those of the core being used. It represents the fraction of the core inside the coil.

Conclusion

To determine the stability of an RF power amplifier, oscillator, or transmitter under harsh conditions, a variable line and fixed attenuator are used to simulate a given VSWR at all phase angles. Below 200 MHz a half-wave adjustable line is cumbersome. This article has described a lumped-constant line stretcher using either variable capacitors or inductors.

The use of moveable slugs eliminates mechanical wear at the electrical grounding point present on the capacitor rotor. For automated testing of production transistors or amplifiers, a frictionless device is necessary.

Today there are few manufacturers still fabricating dual section or butterfly variable capacitors because their use was primarily in electron tube amplifiers.

Reference


1. R.K. Blocksome, "A Binary Stepped Transmission Line," *r.f. design*, July/August 1982, pp. 22-29. □

Announcing SCUC'83

the 5th annual
Satellite Communications Users Conference

August 22-24, 1983

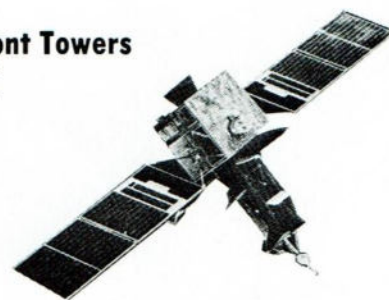**Stouffer's Riverfront Towers
St. Louis, Missouri**



For more information contact:
Satellite Communications magazine

6430 S. Yosemite St.

Englewood, CO 80111 USA

(303) 694-1522

Telex 450726, CRDF ENGL